

Fundamentals of Electronics  
Extract from the Winter Semester Examination (English Translation)  
2 Subjects out of 4

## 2. Subject: MOSFET-Circuits (14 Points)

2.1 Mark the terminals of the transistors with B (Bulk), G (Gate), D (Drain), and S (Source)(Fig. 2.1). Assume  $V_{DD} = 5V$ .

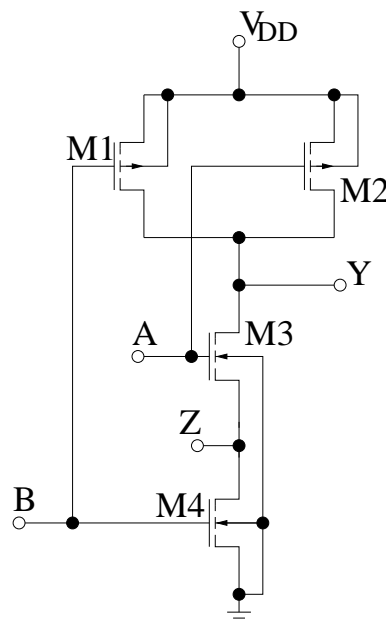


Figure 2.1: Circuit 1

2.2 Which logic function  $Y = Y(A, B)$  is implemented in the circuit represented in Fig. 2.1 implementiert?

Y=
----

2.3 Which is the voltage of the node Z in Fig. 2.1, if  $V_{DD} = 5V$  and the voltages of the nodes A and B are  $5V$  and  $0V$  respectively.

$V_Z =$

2.4 Assume  $V_A = 5V$ ,  $V_B = 0V$ , and  $V_{DD} = 5V$ . Specify the states of the transistors in the circuit represented in Fig. 2.1

- M1:  
- M2:  
- M3:  
- M4:

2.5 Dimension the transistors of the circuit represented in Fig. 2.1 so that the circuit switches two times faster than a symmetrical inverter with the channel length of the NMOS of  $1\mu m$ . Assume  $\mu_n = 2.5\mu_p$ .

- M1: W= L=  
- M2: W= L=  
- M3: W= L=  
- M4: W= L=

### 3. Subject: Bipolar Transistor - Amplifiers (20 Points)

3.1 Evaluate following affirmations:

Yes No Don't Know

The Bipolar Transistor is called bipolar, because it is a symmetrical element, i.e. it is functioning identically when interchanging the collector and the source.

The Bipolar Transistor has an infinite output resistance when considering the Early-Effect.

The Amplifier represented in Figure 3.1 is an Emitter-Follower.

**Note:** One can accumulate maximum 3 points and minimum 0 points. Every question is weighted with 1 point. False answers lead to deduction and 'Don't know' answers are not assessed.

3.2 The following circuit is given:

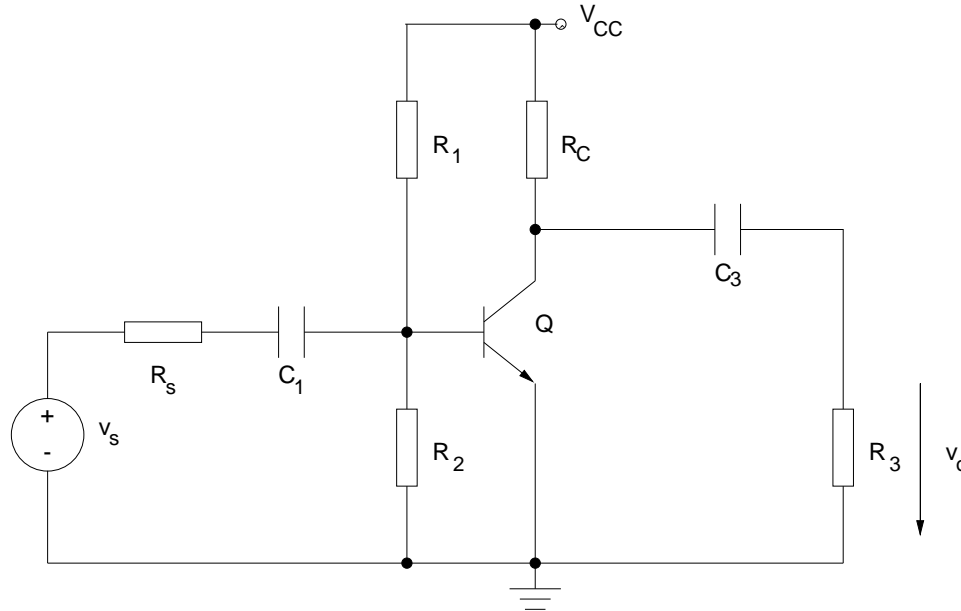


Figure 3.1: Single-Stage Amplifier

Identify the Collector, Base, and Emitter of the Transistor and determine the Q-Point ( $I_C; V_{CE}$ ). Specify  $I_C$  as a function of  $\beta_F, V_{CC}, R_1, R_2$  and  $V_{BE}$ . Assume that the transistor works in the Forward-Active Region and  $V_{BE} = 0.7V$ .  $\beta_F$  is considered to be known and the Early-Effect can be neglected.

3.3 Determine  $g_m = g_m(I_C, V_T)$  from the quadripole description of the transistor (Y-Parameter).

3.4 Draw the Small-Signal model of the circuit. The input-resistance  $r_\pi$  of the transistors is considered to be known. The Early-Effect can be neglected.

3.5 Evaluate the Voltage Amplification of the circuit:

$$A_V(R_S, R_1, R_2, R_3, R_C, g_m, r_\pi) = \frac{v_o}{v_s}.$$